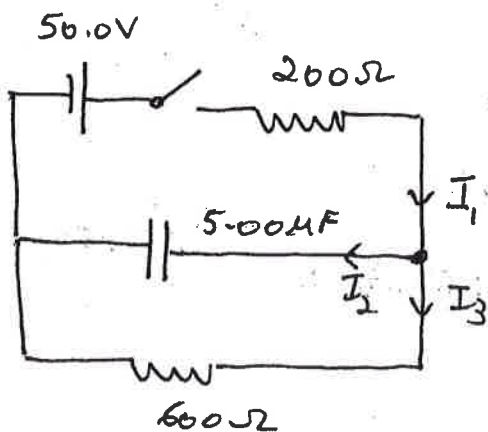


# RC CIRCUIT PROBLEMS

Solution ①

1)



- a) Current through the battery as soon as the switch is closed

$$I_b = \frac{\Delta V_b}{R}$$
$$= \frac{50.0V}{200\Omega} = 0.25A$$

(Capacitor is charging)

- b) Long time later  $\Rightarrow$  Capacitor is charged.

$$I_2 = 0 \quad \text{So} \quad I_b = \frac{50.0V}{600\Omega}$$
$$= 62.5 \text{ mA}$$

- (c) Initially, the current through the  $600\Omega$  resistor = 0A

As the capacitor is charged, the current through the  $600\Omega$  grows. So  $I_{600\Omega} = I_0 [1 - e^{-t/\tau}]$

Since the  $600\Omega$  and the  $200\Omega$  are in parallel,

$$\frac{1}{R} = \frac{1}{600} + \frac{1}{200} \quad R = \frac{600}{4} = 150\Omega$$


$$\text{So } \tau = RC = (150\Omega)(5.00\mu\text{F}) = 0.75\text{s}$$

The current through the  $600 \Omega$  resistor as  $t \rightarrow \infty$

$$I = \frac{\Delta V}{R} = \frac{\Delta V}{R_1 + R_2}$$

$$= 62.5 \text{ mA}$$
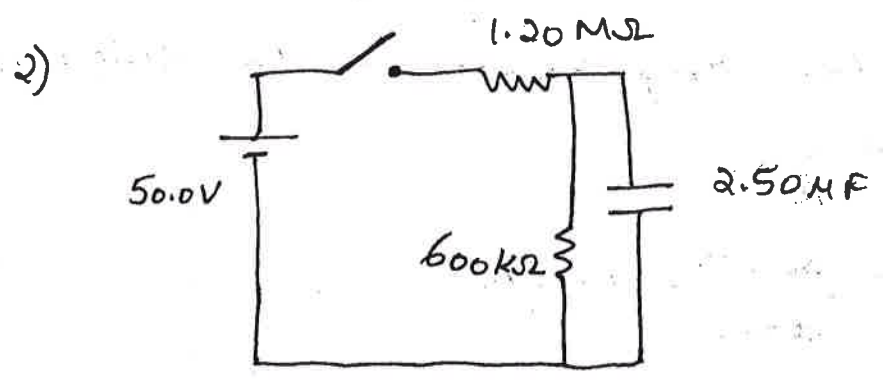
$$I_{600\Omega} = (62.5 \text{ mA}) e^{-t/0.75 \text{ s}}$$



a) Again at  $t=0$   $I_b = \frac{50.0 \text{ V}}{1.20 \text{ M}\Omega} = 41.7 \times 10^{-6} \text{ A}$

b)  $I_b = \frac{50.0 \text{ V}}{600 \cdot 10012} = 83.3 \mu\text{A}$        $\frac{50.0 \text{ V}}{1800 \Omega} = 27.8 \mu\text{A}$        $\frac{50.0 \text{ V}}{1.8 \text{ M}\Omega} = \frac{50.0 \text{ V}}{1.8 \times 10^6 \Omega} = 27.8 \mu\text{A}$

c) Capacitor is charged. As switch is opened, capacitor discharged through the  $600 \text{ k}\Omega$  resistor.

$$I = I_0 e^{-t/RC}$$


$$RC = 600 \times 10^3 \Omega (2.50 \mu\text{F}) = 1.50 \text{ s}$$

$$I_0 = \frac{\Delta V}{R} = \frac{50.0 \text{ V}}{1.20 \times 10^6 \Omega} = 41.7 \times 10^{-6} \text{ A}$$

$$I = (83.3 \mu\text{A}) e^{-t/1.50 \text{ s}}$$

$$\frac{50.0 \text{ V}}{600 \times 10^3 \Omega} = 83.3 \times 10^{-6} = 83.3 \mu\text{A}$$

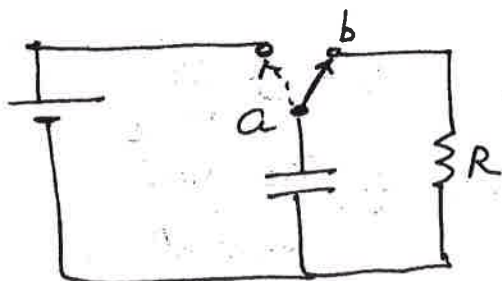3)  $C = 6.00 \mu\text{F}$   $E = 100\text{V}$   $R = 500\Omega$



NOTE original diagram was incorrect.

As the capacitor is fully charged,  $q = C(\Delta V_b)$   
 $= 6.00 \mu\text{F}(100\text{V})$   
 $= 600 \mu\text{C}$

$q = 600 \mu\text{C}$

b) The capacitor starts discharging through the resistor as soon as the switch is thrown to 'b'.

$I = I_0 e^{-t/RC}$

$RC = (500\Omega)(6.00 \mu\text{F})$   
 $= 3 \text{ ms}$

$I_0 = 0.2 \text{ A}$

$I_0 = \frac{E \Delta V}{R}$   
 $= \frac{(6.00 \mu\text{F})(100\text{V})}{500\Omega}$   
 $= 0.2 \text{ A}$

$\tau = RC = 3.0 \text{ ms}$

Charge decreases on the capacitor with time:

$q(t) = Q e^{-t/\tau}$

$= 600 \mu\text{C} e^{-6.00 \text{ ms} / 3 \text{ ms}}$

$q(6 \text{ ms}) = 81.2 \mu\text{C}$

$I_0 = \frac{100\text{V}}{500\Omega} = 0.2 \text{ A}$

4) a) Capacitor is fully charged.

Energy stored in the capacitor

$$U = \frac{1}{2} CV^2$$

$$\text{or } U = \frac{1}{2} \frac{Q^2}{C}$$

$$U = \frac{1}{2} \frac{(600 \mu\text{C})^2}{6.00 \mu\text{F}}$$

$$U = \frac{1}{2} \times \frac{36 \times 10^4 \times 10^{-12}}{6 \times 10^{-6}} = 3 \times 10^{-2} \text{ J}$$

$$U = 3 \times 10^{-2} \text{ J}$$

As the capacitor discharges, its energy stored decreases in time as

$$U = \frac{1}{2C} [Q e^{-t/RC}]^2$$

$$U(t) = \frac{Q^2}{2C} e^{-2t/RC}$$

$$Q = 600 \mu\text{C} \quad C = 6.00 \mu\text{F} \quad RC = 3 \text{ ms}$$

5)  $C = 0.120 \mu\text{F}$   $E = 100 \text{ V}$   $V(4.00 \text{ s}) = \frac{E}{2} = 50.0 \text{ V}$

Capacitor is discharging. So  $\Delta V|_C = \frac{Q}{C}$  is decreasing


$$\Delta V(t) = \frac{1}{C} Q e^{-t/RC}$$

$$\Delta V(4.00 \text{ s}) = 50.0 \text{ V} = \frac{(12.0 \mu\text{C})}{0.120 \mu\text{F}} e^{-\frac{4}{\tau}} \quad \tau = RC$$

$$\Rightarrow \frac{50}{100} = e^{-4/\tau} \quad \ln \frac{1}{2} = -\frac{4}{\tau} \quad \tau = -\frac{4}{\ln(\frac{1}{2})} = 10.915$$

$$RC = \frac{0.12 \mu\text{F}}{10.915} = R(0.12 \mu\text{F}) \quad R = \frac{1.2 \times 10^{-6}}{10.915} = 90.9 \times 10^{-6} \text{ } \Omega \text{ or } 91 \text{ } \mu\Omega$$

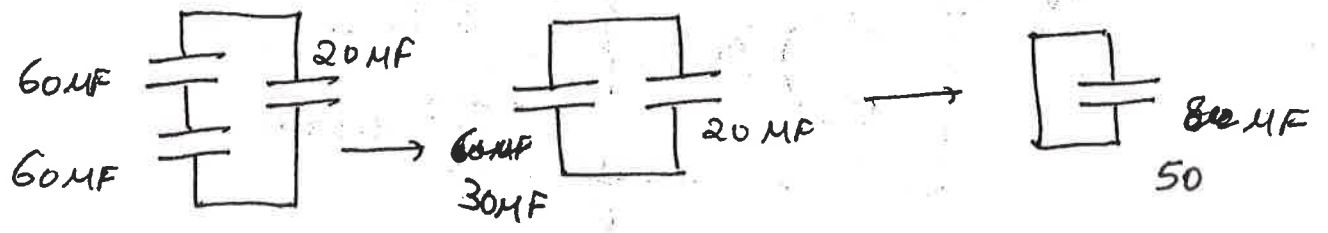
6) The main thing here is to find the time constant.



$$\frac{1}{C} = \frac{1}{60} + \frac{1}{60}$$

$$C = 30 \mu F$$

So  $C_{equivalent} = 50 \mu F$

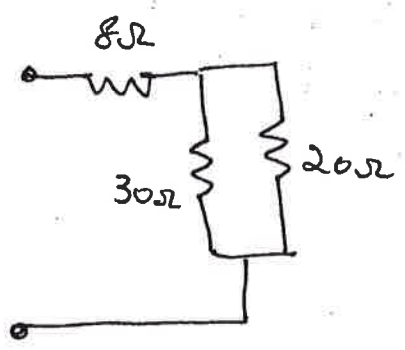


$$\frac{1}{R_{11}} = \frac{1}{30\Omega} + \frac{1}{20\Omega}$$

$$R_{11} = 12\Omega$$

$$\frac{1}{R_{11}} = \frac{1}{8\Omega} + \frac{1}{30\Omega}$$

$$R_{11} = 6.32\Omega$$

$$R = 6.32\Omega + 8\Omega$$

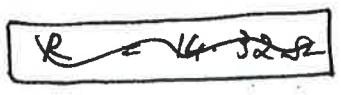

Req<sub>equiv</sub> = 20Ω

So  $R_c = 14.32\Omega$  1.0ms

$$I = I_0 e^{-t/RC}$$

Need: time when  $\frac{I}{I_0} = \frac{1}{2}$

$$t = 0.79 \mu s$$


$$\frac{I}{I_0} = \frac{1}{2} = e^{-t/1 \times 10^{-3} s}$$

$$-0.693 = -\frac{t}{1 \times 10^{-3} s}$$

$$t = 0.693 \text{ ms}$$

7)

a)

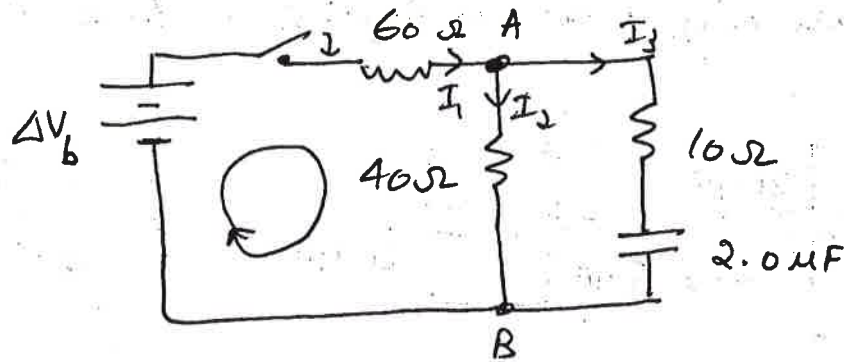

As capacitor is fully charged  $I_3 = 0$

① Using loop rule for the 1st loop

$$\Delta V_b - I_1 (60 \Omega) - I_2 (40 \Omega) = 0$$

② Junction Rule

$$I_1 = I_2 + I_3 = 0$$

$$I_1 = I_2$$

③

$$\Delta V_b = 100 I_1$$

$$I_1 = 1 \text{ A}$$

$$\Rightarrow \Delta V_{AB} = I_1 (40 \Omega) = 40 \text{ V}$$

$$\Delta V_C = \Delta V_{AB} \quad (\text{No voltage drop across } 10 \Omega)$$

$$Q = C \Delta V_C = (2.0 \mu\text{F}) (40 \text{ V})$$

$$Q = 80 \mu\text{C}$$

$$b) \quad RC = \tau = (50 \Omega) (2.0 \mu\text{F}) = 100 \times 10^{-6} \text{ s} = 0.1 \text{ ms}$$

$$\frac{q}{Q} = 0.1 = e^{-t/\tau}$$

$$-\tau \ln(0.1) = t$$

$$t = 0.23 \text{ ms}$$